
VLSI Design : Assignment-1

Monsoon 2024, IIIT Hyderabad (Instructor: Prof. Abhishek Srivastava)

Release date: 11 Aug 2024, Due date : 20 Aug, 2024 (18:00 hrs)

Instructions:

1. Submit your assignment as a single file in pdf format (Name_RollNo.pdf)
 2. Use the given 180 nm technology file for the NGSPICE simulations
 3. Answers should be complete and must be presented in a systematic way with explanation, plots, annotations and netlist
 4. Maximum marks for each question is 10. Bonus marks (10) will be given for a good report
 5. Suggested references:
 - a) Neil H. E. Weste, K. Eshraghian, Principles of CMOS VLSI Design- A Systems Perspective, 2nd Edition, Pearson Education Pvt. Ltd. (**Chapter-2**)
 - b) J. M. Rabaey, A. Chandrakasan, B. Nikolic, Digital Integrated Circuits - A Design Perspective, 2nd Edition, Prentice Hall of India. (**Chapter-3**)
-

1. Install NGSPICE. Run the given net-lists (in tutorial) and observe the results (**No need to submit this part**).
2. Present the derivation for drain current equations I_{DS} of an n channel MOSFET for linear and saturation modes of operation.
3. Discuss the MOS capacitance in various modes (Accumulation, Depletion and Inversion). Give a summary table showing approximate MOS capacitances in cut-off, saturation and linear modes. Give necessary plots to explain.
4. The given Netlist '2_mos_CV_char_aug2024.cir' plots gate capacitance C_{GS} with respect to gate voltage (V_{GS}) of a MOSFET device. Draw the circuit diagram from the netlist and explain how the simulation is used here to estimate C_{GS} .
5. Briefly explain the second order effects in MOSFET - Channel length modulation, velocity saturation, mobility degradation, drain induced barrier lowering (DIBL), body-effect and sub-threshold conduction.
6. Plot I_D vs V_{GS} for $\frac{1.8\mu}{0.18\mu}$ NMOS transistor and estimate its V_T from the graph for the following cases :
 - (a) $V_{DS} = 50$ mV and V_{GS} is swept from 0 to 1.8 V in a step of 0.1 V
 - (b) $V_{DS} = 1.8$ V and V_{GS} is swept from 0 to 1.8 V in a step of 0.1 V
 - (c) Do you observe any difference in V_T values in case (a) and (b) ? If yes, explain why.
7. From the simple MOS models discussed in class, find out the technology parameter μC_{ox} and V_T for NMOS and PMOS devices with the help of simulations for i) Body to source voltage (V_{BS}) of 0V, ii) $V_{BS} = 900$ mV and ii) $V_{BS} = -900$ mV . Do you observe any difference in V_T for the three cases? Explain.
8. Plot $I_D - V_{DS}$ for the two cases shown in figures 1(a) and (b). Explain why a W/2L transistor does not behave in exactly the same way as a series combination of two W/L transistors for small values of L.

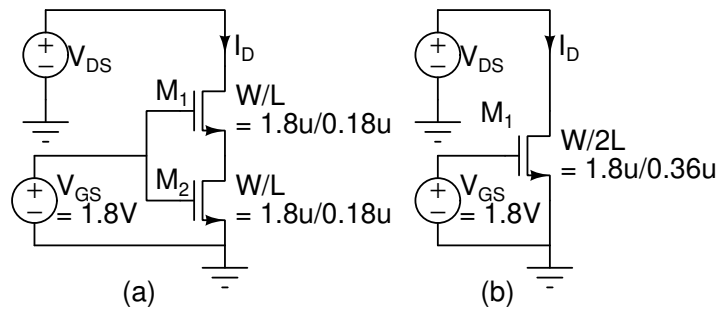


Figure 1

9. Consider the circuits shown in figures 2(a) and (b). Find the peak I_{ON} and average I_{OFF} for $W = 1.8\mu\text{m}$, $W = 3.6\mu\text{m}$, $W = 18\mu\text{m}$, $W = 36\mu\text{m}$. (Give plot snapshots and a table of I_{ON} and I_{OFF} for different W .) Do I_{ON} and I_{OFF} scale linearly with respect to W , comment.

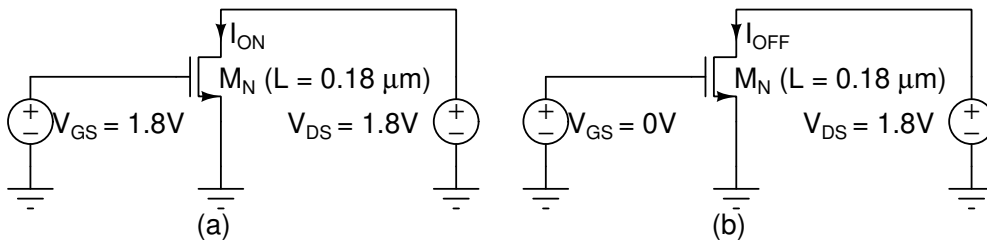


Figure 2

10. Consider the schematic shown in figure 3. Switch 'SW' is closed at time $t=0$.

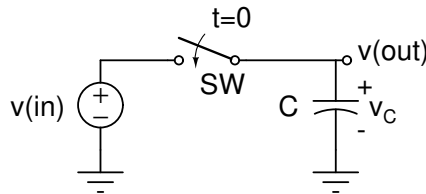


Figure 3

- (a) Replace the switch 'SW' by an NMOS ($W/L = \frac{1.8\mu}{0.18\mu}$) and plot $v(\text{out})$, when i) $v_c(0^-) = 0\text{V}$ and $v(\text{in}) = 1.8\text{V}$, ii) $v_c(0^-) = 1.8\text{V}$ and $v(\text{in}) = 0\text{V}$. Do you get exact same voltage at output as at input in steady state for both the cases. Comment for both the cases with reasons for difference (if any).
- (b) Replace the switch 'SW' by a PMOS ($W/L = \frac{1.8\mu}{0.18\mu}$) and plot $v(\text{out})$, when i) $v_c(0^-) = 0\text{V}$ and $v(\text{in}) = 1.8\text{V}$, ii) $v_c(0^-) = 1.8\text{V}$ and $v(\text{in}) = 0\text{V}$. Do you get exact same voltage at output as at input in steady state for both the cases. Comment for both the cases with reasons for difference (if any).

(Hint : use `.ic v(node-name)=value` to set initial condition at a node before `.control` in your netlist)

11. Write a netlist for the circuit shown in figure 4. Remember to specify the AS, AD and PS, PD parameters for the transistors.

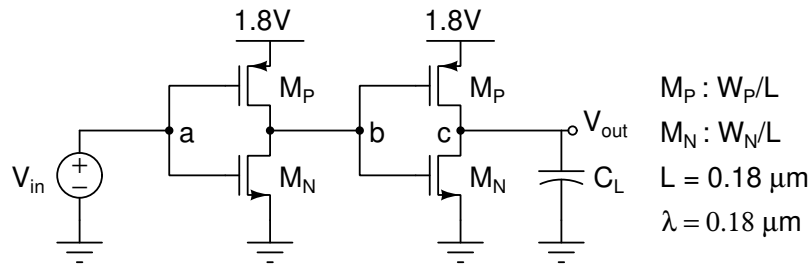


Figure 4

Plot V_{out} with respect to time and calculate the propagation delay between input and output (t_{pd}) and tabulate them for the following cases:

Given: V_{in} (vin a 0 pulse 0 1.8 0ns 100ps 100ps 9.9ns 20ns)

- (a) $C_L = 100 \text{ fF}$, $W_n = 1.8 \mu\text{m}$ $W_p = 2.5 \times W_n$
- (b) $C_L = 500 \text{ fF}$ $W_n = 1.8 \mu\text{m}$ $W_p = 2.5 \times W_n$
- (c) $C_L = 500 \text{ fF}$ $W_n = 9 \mu\text{m}$ $W_p = 2.5 \times W_n$.
- (d) From the delay table, comment how the scaling up of transistor widths affects the propagation delays.

Note: Delay = (rise-time + fall-time)/2, where rise-time is defined as the delay between rising output and corresponding falling input when both are at their 50% values. Similarly fall-time is defined as the delay between falling output and corresponding rising input when both are at their 50% values.